

EECS 150 - Components and Design Techniques for Digital Systems

Lec 26 – CRCs, LFSRs (and a little power)

David Culler
Electrical Engineering and Computer Sciences
University of California, Berkeley

<http://www.eecs.berkeley.edu/~culler>
<http://www-inst.eecs.berkeley.edu/~cs150>

1

Review

- **Concept of error coding**
 - Add a few extra bits (enlarges the space of values) that carry information about all the bits
 - Detect: Simple function to check of entire data+check received correctly
 - » Small subset of the space of possible values
 - Correct: Algorithm for locating nearest valid symbol
- **Hamming codes**
 - Selective use of parity functions
 - Distance + # bit flips
 - Parity: XOR of the bits => single error detection
 - SECDED
 - » $\text{data bits} + p + 1 < 2^p$

2


Outline

- Introduce LFSR as fancy counter
- Practice of Cyclic Redundancy Checks
 - Burst errors in networks, disks, etc.
- Theory of LFSRs
- Power

3


Linear Feedback Shift Registers (LFSRs)

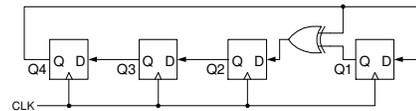- These are n-bit counters exhibiting *pseudo-random* behavior.
- Built from simple shift-registers with a small number of xor gates.
- Used for:
 - random number generation
 - counters
 - error checking and correction
- Advantages:
 - very little hardware
 - high speed operation
- Example 4-bit LFSR:



4

4-bit LFSR

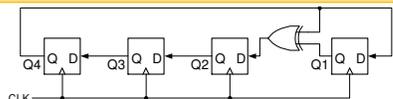

- Circuit counts through $2^n - 1$ different non-zero bit patterns.
- Left most bit determines shift or more complex operation
- Can build a similar circuit with any number of FFs, may need more xor gates.
- In general, with n flip-flops, $2^n - 1$ different non-zero bit patterns.
- (Intuitively, this is a counter that wraps around many times and in a strange way.)

```

0001
0010
0100
1000
0011
0110
1100
1011
0101
1010
0111
1110
1111
1101
1001
0001
  
```

xor 0 0 0 0 0
xor 0 0 1 1 0
xor 0 0 0 0 0
xor 0 1 1 0 0
xor 0 0 0 0 0
xor 1 0 0 1 1
xor 0 0 1 1 0
xor 0 0 0 0 0
xor 0 1 1 1 0
xor 0 0 0 0 0
xor 1 1 0 0 0
xor 1 0 0 1 1
xor 0 1 0 1 1

5

Applications of LFSRs

- **Performance:**
 - In general, xors are only ever 2-input and never connect in series.
 - Therefore the minimum clock period for these circuits is:
 - $T > T_{2\text{-input-xor}} + \text{clock overhead}$
 - Very little latency, and independent of n!
- This can be used as a **fast counter**, if the particular sequence of count values is not important.
 - Example: micro-code micro-pc
- Can be used as a **random number generator**.
 - Sequence is a pseudo-random sequence:
 - » numbers appear in a random sequence
 - » repeats every $2^n - 1$ patterns
 - Random numbers useful in:
 - » computer graphics
 - » cryptography
 - » automatic testing
- Used for error detection and correction
 - » CRC (cyclic redundancy codes)
 - » ethernet uses them

6


Concept: Redundant Check

- Send a message M and a “check” word C
- Simple function on $\langle M, C \rangle$ to determine if both received correctly (with high probability)
- Example: XOR all the bytes in M and append the “checksum” byte, C , at the end
 - Receiver XORs $\langle M, C \rangle$
 - What should result be?
 - What errors are caught?




7

Example: TCP Checksum

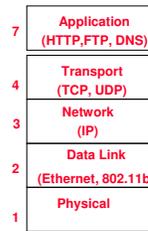



TCP Packet Format

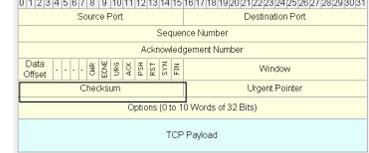

- TCP Checksum a 16-bit **checksum**, consisting of the **one's complement** of the **one's complement sum** of the contents of the TCP segment header and data, is computed by a sender, and included in a segment transmission. (note end-around carry)
- Summing all the words, including the checksum word, should yield zero

8

Example: Ethernet CRC-32

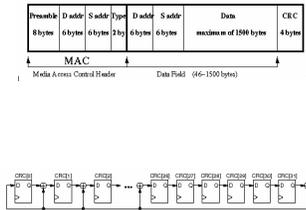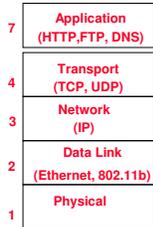

9

CRC concept


- I have a msg polynomial $M(x)$ of degree m
- We both have a generator poly $G(x)$ of degree n
- Let $r(x) = \text{remainder of } M(x) \cdot x^n / G(x)$
 - $M(x) \cdot x^n = G(x) \cdot p(x) + r(x)$
 - $r(x)$ is of degree n
- What is $(M(x) \cdot x^n - r(x)) / G(x)$? n bits of zero at the end
- So I send you $M(x) \cdot x^n - r(x)$ tack on n bits of remainder instead of the zeros
 - $m+n$ degree polynomial
 - You divide by $G(x)$ to check
 - $M(x)$ is just the m most significant coefficients, $r(x)$ the lower m
- n -bit Message is viewed as coefficients of n -degree polynomial over binary numbers

10

Announcements

- Reading
 - XILINX IEEE 802.3 Cyclic Redundancy Check (pages 1-3)
 - http://ftp.rocksoft.com/papers/crc_v3.txt
- Final on 12/15
- What's Going on in EECS?
 - Towards simulation of a Digital Human
 - Yelick: Simulation of the Human Heart Using the Immersed Boundary Method on Parallel Machines

Digital Human Today: Imaging

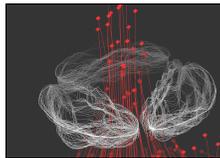

11

Galois Fields - the theory behind LFSRs

- LFSR circuits performs multiplication on a *field*.
- A field is defined as a *set* with the following:
 - two operations defined on it:
 - » “addition” and “multiplication”
 - closed under these operations
 - associative and distributive laws hold
 - additive and multiplicative identity elements
 - additive inverse for every element
 - multiplicative inverse for every non-zero element
- Example fields:
 - set of rational numbers
 - set of real numbers
 - set of integers is *not* a field (why?)
- Finite fields are called *Galois fields*.
- Example:
 - Binary numbers 0,1 with XOR as “addition” and AND as “multiplication”.
 - Called $GF(2)$.

- $0+1 = 1$
- $1+1 = 0$
- $0-1 = ?$
- $1-1 = ?$

12

Galois Fields - The theory behind LFSRs

- Consider *polynomials* whose coefficients come from GF(2).
- Each term of the form x^n is either present or absent.
- Examples: $0, 1, x, x^2,$ and $x^7 + x^6 + 1$
 $= 1 \cdot x^7 + 1 \cdot x^6 + 0 \cdot x^5 + 0 \cdot x^4 + 0 \cdot x^3 + 0 \cdot x^2 + 0 \cdot x^1 + 1 \cdot x^0$
- With addition and multiplication these form a field:
- "Add": XOR each element individually with no carry:

$$\begin{array}{r} x^4 + x^3 + + x + 1 \\ + x^4 + + x^2 + x \\ \hline x^3 + x^2 + + 1 \end{array}$$
- "Multiply": multiplying by x^n is like shifting to the left.

$$\begin{array}{r} x^2 + x + 1 \\ \times + x + 1 \\ \hline x^3 + x^2 + x \\ + x + 1 \\ \hline x^3 + x^2 + x + 1 \end{array}$$

13

So what about division (mod)

$$\frac{x^4 + x^2}{x} = x^3 + x \text{ with remainder } 0$$


$$\frac{x^4 + x^2 + 1}{x + 1} = x^3 + x^2 \text{ with remainder } 1$$

$$\begin{array}{r} x^3 + x^2 + 0x + 0 \\ X + 1 \overline{) x^4 + 0x^3 + x^2 + 0x + 1} \\ \underline{x^4 + x^3} \\ x^3 + x^2 \\ \underline{x^3 + x^2} \\ 0x^2 + 0x + 1 \\ \underline{0x^2 + 0x} \\ 0x + 1 \\ \underline{0x + 1} \\ \text{Remainder } 1 \end{array}$$

14

Polynomial division

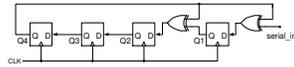
$$\begin{array}{r} 0000101 \\ 10011 \overline{) 10110010000} \\ \underline{10011} \\ 01010 \\ \underline{01010} \\ 00000 \end{array}$$



- When MSB is zero, just shift left, bringing in next bit
- When MSB is 1, XOR with divisor and shift!

15

CRC encoding

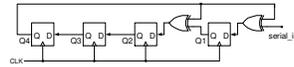


0	0	0	0	0	10110010000
0	0	0	0	1	0110010000
0	0	1	0	0	110010000
0	1	0	1	0	10010000
1	0	1	1	0	0010000
0	1	0	1	0	010000
1	0	1	0	0	10000
0	1	1	0	0	0000
1	1	0	0	0	000
1	0	1	1	0	00
0	1	0	1	0	0
1	0	1	0	0	

Message sent:

10110011010

16

CRC decoding

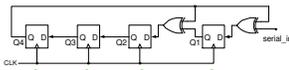

0	0	0	0	0	10110011010
0	0	0	0	1	0110011010
0	0	1	0	0	110011010
0	1	0	1	0	10011010
1	0	1	1	0	0011010
0	1	0	1	0	011010
1	0	1	0	0	1010
0	1	1	0	1	010
1	0	0	1	0	10
0	0	0	0	0	0
0	0	0	0	0	

17

Galois Fields - The theory behind LFSRs

- These polynomials form a *Galois (finite) field* if we take the results of this multiplication modulo a prime polynomial $p(x)$.
 - A prime polynomial is one that cannot be written as the product of two non-trivial polynomials $q(x)r(x)$
 - Perform modulo operation by subtracting a (polynomial) multiple of $p(x)$ from the result. If the multiple is 1, this corresponds to XOR-ing the result with $p(x)$.
- For any degree, there exists at least one prime polynomial.
- With it we can form $GF(2^n)$
- Additionally, ...
- Every Galois field has a primitive element, α , such that all non-zero elements of the field can be expressed as a power of α . By raising α to powers (modulo $p(x)$), all non-zero field elements can be formed.
- Certain choices of $p(x)$ make the simple polynomial x the primitive element. These polynomials are called *primitive*, and one exists for every degree.
- For example, $x^4 + x + 1$ is primitive. So $\alpha = x$ is a primitive element and successive powers of α will generate all non-zero elements of $GF(16)$. *Example on next slide.*

18

Galois Fields – Primitives

$$\begin{aligned} \alpha^0 &= 1 \\ \alpha^1 &= x \\ \alpha^2 &= x^2 \\ \alpha^3 &= x^3 \\ \alpha^4 &= x + 1 \\ \alpha^5 &= x^2 + x \\ \alpha^6 &= x^3 + x^2 \\ \alpha^7 &= x^3 + x + 1 \\ \alpha^8 &= x^2 + x + 1 \\ \alpha^9 &= x^3 + x \\ \alpha^{10} &= x^2 + x + 1 \\ \alpha^{11} &= x^3 + x^2 + x \\ \alpha^{12} &= x^3 + x^2 + x + 1 \\ \alpha^{13} &= x^3 + x^2 + 1 \\ \alpha^{14} &= x^3 + x + 1 \\ \alpha^{15} &= 1 \end{aligned}$$

• Note this pattern of coefficients matches the bits from our 4-bit LFSR example.

$$\begin{aligned} \alpha^4 &= x^4 \bmod x^4 + x + 1 \\ &= x^4 \text{ xor } x^4 + x + 1 \\ &= x + 1 \end{aligned}$$

• In general finding primitive polynomials is difficult. Most people just look them up in a table, such as:

19

Primitive Polynomials

$x^2 + x + 1$	$x^{12} + x^6 + x^4 + x + 1$	$x^{22} + x + 1$
$x^3 + x + 1$	$x^{13} + x^4 + x^3 + x + 1$	$x^{23} + x^5 + 1$
$x^4 + x + 1$	$x^{14} + x^{10} + x^6 + x + 1$	$x^{24} + x^7 + x^2 + x + 1$
$x^5 + x^2 + 1$	$x^{15} + x + 1$	$x^{25} + x^3 + 1$
$x^6 + x + 1$	$x^{16} + x^{12} + x^3 + x + 1$	$x^{26} + x^6 + x^2 + x + 1$
$x^7 + x^3 + 1$	$x^{17} + x^3 + 1$	$x^{27} + x^5 + x^2 + x + 1$
$x^8 + x^4 + x^3 + x^2 + 1$	$x^{18} + x^7 + 1$	$x^{28} + x^3 + 1$
$x^9 + x^4 + 1$	$x^{19} + x^5 + x^2 + x + 1$	$x^{29} + x + 1$
$x^{10} + x^3 + 1$	$x^{20} + x^3 + 1$	$x^{30} + x^6 + x^4 + x + 1$
$x^{11} + x^2 + 1$	$x^{21} + x^2 + 1$	$x^{31} + x^3 + 1$
		$x^{32} + x^7 + x^6 + x^2 + 1$

Galois Field

Multiplication by x

\Leftrightarrow shift left

Taking the result mod $p(x) \Leftrightarrow$ XOR-ing with the coefficients of $p(x)$ when the most significant coefficient is 1.



Obtaining all $2^n - 1$ non-zero elements by evaluating x^k for $k = 1, \dots, 2^n - 1$

elements by evaluating x^k for $k = 1, \dots, 2^n - 1$

20

Building an LFSR from a Primitive Poly

- For k -bit LFSR number the flip-flops with FF1 on the right.
- The feedback path comes from the Q output of the leftmost FF.
- Find the primitive polynomial of the form $x^k + \dots + 1$.
- The $x^0 = 1$ term corresponds to connecting the feedback directly to the D input of FF 1.
- Each term of the form x^n corresponds to connecting an xor between FF n and $n+1$.
- 4-bit example, uses $x^4 + x + 1$
 - $x^4 \Leftrightarrow$ FF4's Q output
 - $x \Leftrightarrow$ xor between FF1 and FF2
 - $1 \Leftrightarrow$ FF1's D input
- To build an 8-bit LFSR, use the primitive polynomial $x^8 + x^4 + x^3 + x^2 + 1$ and connect xors between FF2 and FF3, FF3 and FF4, and FF4 and FF5.

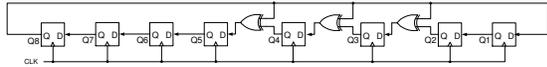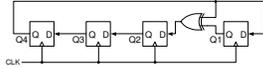

21

Generating Polynomials

- CRC-16:** $G(x) = x^{16} + x^{15} + x^2 + 1$
 - detects single and double bit errors
 - All errors with an odd number of bits
 - Burst errors of length 16 or less
 - Most errors for longer bursts
- CRC-32:** $G(x) = x^{32} + x^{26} + x^{23} + x^{22} + x^{16} + x^{12} + x^{11} + x^{10} + x^8 + x^7 + x^5 + x^4 + x^2 + x + 1$
 - Used in ethernet
 - Also 32 bits of 1 added on front of the message
 - Initialize the LFSR to all 1s

22

POWER

23

Motivation

Why should a digital designer care about power consumption?

- Portable devices:**
 - handhelds, laptops, phones, MP3 players, cameras, ... all need to run for extended periods on small batteries without recharging
 - Devices that need regular recharging or large heavy batteries will lose out to those that don't.
- Power consumption important even in "tethered" devices.**
 - System cost tracks power consumption:
 - power supplies, distribution, heat removal
 - power conservation, environmental concerns
 - In a span of 10 years we have gone from designing without concern for power consumption to (in many cases) designing with power consumption as the primary design constraint!

24

Battery Technology

- Battery technology has moved very slowly
 - Moore's law does not seem to apply
- Li-Ion and NiMH still the dominate technologies
- Batteries still contribute significant to the weight of mobile devices



Nokia 61xx - 33%



Handspring PDA - 10%



Toshiba Portege 3110 laptop - 20%

25

Basics

- Power supply provides energy for charging and discharging wires and transistor gates. The energy supplied is stored and dissipated as heat.

$$P \equiv dw/dt \quad \text{Power: Rate of work being done w.r.t time. Rate of energy being used.}$$

Units: $P = E/\Delta t$ Watts = Joules/seconds

- If a differential amount of charge dq is given a differential increase in energy dw , the potential of the charge is increased by: $V = dw/dq$
- By definition of current: $I = dq/dt$

$$dw/dt = \frac{dw}{dq} \times \frac{dq}{dt} = P = V \times I \quad \text{A very practical formulation!}$$

$$w = \int_{-\infty}^t P dt \quad \text{total energy} \quad \text{If we would like to know total energy}$$

26

Basics

- Warning!** In everyday language, the term "power" is used incorrectly in place of "energy."
- Power is **not** energy.
- Power is **not** something you can run out of.
- Power can **not** be lost or used up.
- It is **not** a thing, it is merely a rate.
- It can **not** be put into a battery any more than velocity can be put in the gas tank of a car.

27

Metrics

How do we measure and compare power consumption?

- One popular metric for microprocessors is: MIPS/watt
 - MIPS, millions of instructions per second.
 - Typical modern value?
 - Watt, standard unit of power consumption.
 - Typical value for modern processor?
 - MIPS/watt is reflective of the tradeoff between performance and power. Increasing performance requires increasing power.
 - Problem with "MIPS/watt"
 - MIPS/watt values are typically not independent of MIPS
 - techniques exist to achieve very high MIPS/watt values, but at very low absolute MIPS (used in watches)
 - Metric only relevant for comparing processors with a similar performance.
 - One solution, MIPS²/watt. Puts more weight on performance.

28

Metrics


- How does MIPS/watt relate to energy?
 - Average power consumption = energy / time
- $$\text{MIPS/watt} = \text{instructions/sec} / \text{joules/sec} = \text{instructions/joule}$$
- therefore an equivalent metric (reciprocal) is energy per operation (E/op)
- E/op is more general - applies to more than processors
 - also, usually more relevant, as batteries life is limited by total energy draw.
 - This metric gives us a measure to use to compare two alternative implementations of a particular function.

29

Power in CMOS

Switching Energy:

energy used to switch a node

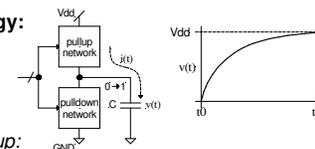

Calculate energy dissipated in pullup:

$$E_{sw} = \int_{t_0}^{t_1} P(t) dt = \int_{t_0}^{t_1} (V_{dd} - v) \cdot i(t) dt = \int_{t_0}^{t_1} (V_{dd} - v) \cdot c (dv/dt) dt =$$

$$= cV_{dd} \int_{t_0}^{t_1} dv - c \int_{t_0}^{t_1} v \cdot dv = cV_{dd}^2 - 1/2 cV_{dd}^2 = 1/2 cV_{dd}^2$$

Energy supplied
Energy stored
Energy dissipated


An equal amount of energy is dissipated on pulldown.

30

Switching Power

Gate power consumption:

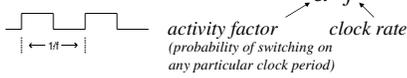- Assume a gate output is switching its output at a rate of:



$$P_{avg} = E/\Delta t = \text{switching rate} \cdot E_{sw}$$

Therefore:

$$P_{avg} = \alpha \cdot f \cdot 1/2 c V_{dd}^2$$

Chip/circuit power consumption:


$$P_{avg} = n \cdot \alpha_{avg} \cdot f \cdot 1/2 c_{avg} V_{dd}^2$$

number of nodes (or gates)


31

Other Sources of Energy Consumption


"Short Circuit" Current:

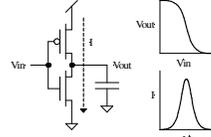

Junction Diode Leakage:

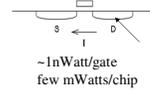

Device Ids Leakage:

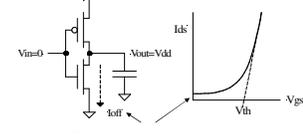

32

Controlling Energy Consumption

What control do you have as a designer?

- Largest contributing component to CMOS power consumption is switching power:

$$P_{avg} = n \cdot \alpha_{avg} \cdot f \cdot 1/2 c_{avg} V_{dd}^2$$

- Factors influencing power consumption:
n: total number of nodes in circuit

α : activity factor (probability of each node switching)

f: clock frequency (does this effect energy consumption?)




V_{dd} : power supply voltage

- What control do you have over each factor?
- How does each effect the total Energy?

33

Power / Cost / Performance

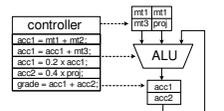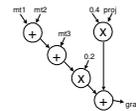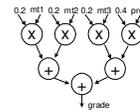- Parallelism to trade cost for performance. As we trade cost for performance what happens to energy?



- The lowest energy consumer is the solution that minimizes cost without time multiplexing operations.

34